

ECE 223 LAB EXPERIMENT 1

Experiment Part:

- 1) Construct an Inverter circuit and draw its truth table.
- 2) Construct an AND gate circuit and draw its truth table.
- 3) Construct an OR gate circuit and draw its truth table.

Show every step to your instructor.