

ECE 223 LAB EXPERIMENT 2

Preparation Part:

- 1) Construct the truth table of below digital design.

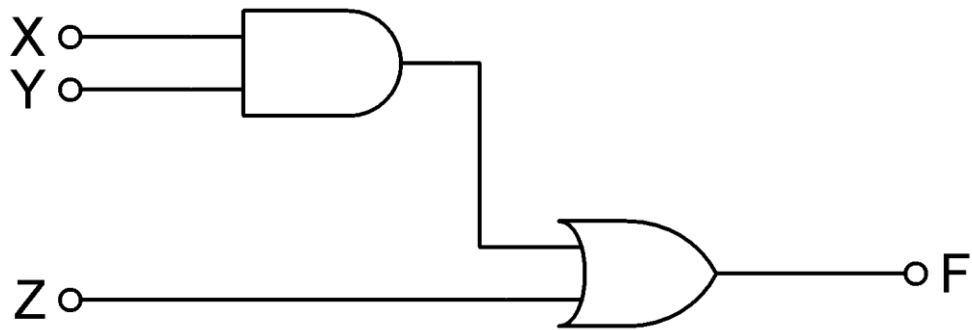


Figure-1

- 2) Construct the truth table of below digital design.

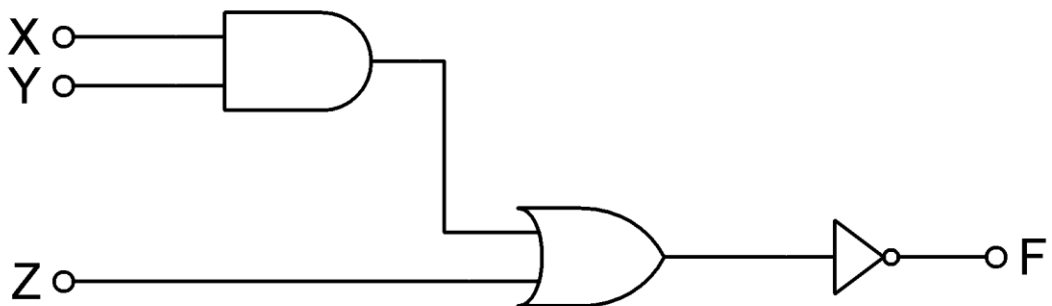


Figure-2

Experiment Part:

1. Construct the circuit in Figure-1. Show the results.
2. Construct the circuit in Figure-2. Show the results.