

ECE 223 LAB EXPERIMENT 4

Preparation Part:

- a) Implement a XOR gate by only using inverter and NAND gates. Draw truth table and logic circuit.
- b) Implement $F = B'C' + BC + ABC$ by only using inverter and NAND gates. Draw truth table and logic circuit.
- c) Implement a XOR gate by only using inverter and NOR gates. Draw truth table and logic circuit.
- d) Implement 3 input AND gate by only using inverter and NOR gates. Draw truth table and logic circuit.

Experiment Part:

- 1) Set up the logic circuit a in preparation part and show the result to your instructor.
- 2) Set up the logic circuit d in preparation part and show the result to your instructor.

